# Chapter 2 Interconnect Analysis



## Outline

## Delay models

- > Review of Elmore Delay
- > Second Order Analysis (S2P algorithm)
- > Gate delay

#### **Review of Elmore Delay**

50% Delay for lumped RC model





How about more complex circuits?





Elmore delay at node i is

 $\begin{aligned} \mathbf{T}_{\text{Di}} &= 0.69(\mathbf{R}_{\text{i}1}\mathcal{C}_1 + \mathbf{R}_{\text{i}2}\mathcal{C}_2 + \mathbf{R}_{\text{i}3}\mathcal{C}_3 + \mathbf{R}_{\text{i}4}\mathcal{C}_4 + \mathbf{R}_{\text{i}i}\mathcal{C}_i) \\ &= 0.69(\mathbf{R}_1\mathcal{C}_1 + \mathbf{R}_1\mathcal{C}_2 + (\mathbf{R}_1 + \mathbf{R}_3)\mathcal{C}_3 + (\mathbf{R}_1 + \mathbf{R}_3)\mathcal{C}_4 + (\mathbf{R}_1 + \mathbf{R}_3 + \mathbf{R}_i)\mathcal{C}_i) \\ &= 0.69(\mathbf{R}_1(\mathcal{C}_1 + \mathcal{C}_2 + \mathcal{C}_3 + \mathcal{C}_4 + \mathcal{C}_i) + \mathbf{R}_3(\mathcal{C}_3 + \mathcal{C}_4 + \mathcal{C}_i) + \mathbf{R}_i\mathcal{C}_i) \end{aligned}$ 

### Elmore Delay Approximation



The Elmore delay is the metric of choice for performancedriven design applications due to its simple, explicit form and ease with which sensitivity information can be calculated

However, for deep submicron technologies (DSM), the accuracy of the Elmore delay is insufficient

## Outline

## Delay models

- > Review of Elmore Delay
- Second Order Analysis (S2P algorithm)
- > Gate delay

#### Alternative solution: S2P Algorithm

Second Order Analysis (Stable 2-Pole Delay Algorithm)

#### General Idea: MOR

Original RC network:  $H(s), Y(s) = \sum_{n=1}^{q} \frac{k_n}{s - p_n} + k_0$ 2 poles Model: (Model Order Reduction: AWE)  $h(s) = \frac{b_0 + b_1 s}{1 + a_1 s + a_2 s^2} = \frac{k_1}{s - p_1} + \frac{k_2}{s - p_2}$ Generate the time domain single from 2P model: eg: Impulse Response:  $\hat{h}(t) = (k_1 e^{p_1 t} + k_2 e^{p_2 t}) \times u(t)$ 

*Emrah Acar, Altan Odabasioglu, Mustafa Celik, and Lawrence T. Pileggi.* 1999. "S2P: A Stable 2-Pole RC Delay and Coupling Noise Metric". *In Proceedings of the Ninth Great Lakes Symposium on VLSI(GLS '99).* 

#### Moments of H(s)

#### Moments of H(s) are coefficients of the Taylor's Expansion of H(s) about s=0

$$H(s) = H_0 + s \frac{d}{ds} H(s) \Big|_{s=0} + s^2 \frac{1}{2!} \frac{d^2}{ds^2} H(s) \Big|_{s=0} + s^3 \frac{1}{3!} \frac{d^3}{ds^3} H(s) \Big|_{s=0} + \dots$$
$$= m^{(0)} + sm^{(1)} + s^2 m^{(2)} + s^3 m^{(3)} + \dots$$

$$m^{(j)} = \frac{1}{j!} \frac{d^j}{ds^j} H(s) \Big|_{s=0}$$

#### **Driving Point Admittance**

Let Y(s) be an driving point admittance function of a general RC circuit. Consider its representation in terms poles and residues

$$Y(s) = \sum_{n=1}^{q} \frac{k_n}{s - p_n} + k_0 \quad \text{where } q \text{ is the exact order of the circuit}$$

Moments of Y(s) can be written as:

$$m_i = \sum_{n=1}^q \frac{k_n}{p_n^{i+1}} \qquad i > 0$$

#### S2P Algorithm

#### Compute m1, m2, m3 and m4 for Y(s)

Find the two poles at the driving point admittance as follows:

$$a_1 = \frac{m_2 m_3 - m_1 m_4}{m_1 m_3 - m_2^2}, \qquad a_2 = \frac{m_2 m_4 - m_3^2}{m_1 m_3 - m_2^2} \qquad p_1 = \frac{(-a_1 + \sqrt{a_1^2 - 4a_2})}{2a_2} \qquad p_2 = \frac{(-a_1 - \sqrt{a_1^2 - 4a_2})}{2a_2}$$

To match the voltage moments at the response nodes, choose

$$k_2 = \frac{(m_0^*/p_1 - m_1^*)}{1/p_2 - 1/p_1} p_2 \qquad k_1 = (-m_0^* - k_2/p_2) p_1$$

and the S2P approximation is then expressed as:

$$\hat{h}(s) = \frac{k_1}{s - p_1} + \frac{k_2}{s - p_2}$$
Note that  $m_0^*$  and  $m_1^*$   
are the moments of H(s)  
 $m_0^*$  is the Elmore delay.

*Emrah Acar, Altan Odabasioglu, Mustafa Celik, and Lawrence T. Pileggi.* 1999. "S2P: A Stable 2-Pole RC Delay and Coupling Noise Metric". *In Proceedings of the Ninth Great Lakes Symposium on VLSI(GLS '99).* 

#### S2P Vs. Elmore Delay



## Outline

## Delay models

- > Review of Elmore Delay
- > Second Order Analysis (S2P algorithm)
- Gate delay

## Gate Delay

### Overall flow of delay calculation



$$Delay_{AC} = Delay_{AB} + Delay_{BC}$$

Delay<sub>AB</sub>: Gate delay Delay<sub>BC</sub>: RC network delay

#### General Model of a Gate



### Definitions



## Gate Delay and Output Transition Time



*Gate* 
$$Delay = f(T_{in}, C_{load})$$

*Output* Transition Time =  $f(T_{in}, C_{load})$ 

The gate delay and the output transition time are functions of both input slew and the output load

#### Output Response for Different Loads



## ASIC Cell Delay Model

- Three approaches for gate propagation delay computation are based on:
  - Delay look-up tables
  - K-factor approximation
    - Effective capacitance
- Delay look-up table is currently in wide use especially in the ASIC design flow
- Effective capacitance promises to be more accurate when the load is not purely capacitive

### Table Look-Up Method



• What is the delay when  $Cl_{oad}$  is 505f F and  $T_{in}$  is 90pS?

### K-factor Approximation



We can fit the output transition time v.s. input transition time and output load as a polynomial function, e.g.

 $T_{output} = k_1 + k_2 C_{load} + T_{in}(k_3 + k_4 C_{load}) - k_5 C_{load}^2$ 

A similar equation gives the gate delay

How to calculate the C<sub>load</sub>??



*Gate* 
$$Delay = f(T_{in}, C_{load})$$

*Output* Transition  $Time = f(T_{in}, C_{load})$ 

The gate delay and the output transition time are functions of both input slew and the output load

#### Second-order RC- $\pi$ Model

Using Taylor Expansion around s = 0



#### Second-order RC- $\pi$ Model (Cont'd)



*Gate*  $Delay = f(T_{in}, C_1, R_{\pi}, C_2)$ 

 This equation requires creation of a fourdimensional table to achieve high accuracy

 This is however costly in terms of memory space and computational requirements

### Effective Capacitance Approach



The "Effective Capacitance" approach attempts to find a single capacitance value that can be replaced instead of the RC- $\pi$  load such that both circuits behave similarly during transition

What's the value of Ceff, C1+C2???

#### Output Response for Effective Capacitance



### Effective Capacitance (Cont'd)



### Effective Capacitance (Cont'd)



- $C_{eff} = C_1 + kC_2$  0<k<1
- Because of the shielding effect of the interconnect resistance, the driver will only "see" a portion of the far-end capacitance C2



#### Effective Capacitance for Different Resistive Shielding



# Macy's Approach



Assumption: If two circuits have the same loads and output transition times, then their effective capacitances are the same

=> the effective capacitance is only a function of the output transition time and the load

*R. Macys and S. McCormick, "A New Algorithm for Computing the "Effective Capacitance" in Deep Sub-micron Circuits", Custom Integrated Circuits Conference 1998, pp. 313-316* 

## Macy's Iterative Solution

- 1. Compute  $\alpha$  from  $C_1$  and  $C_2$
- 2. Choose an initial value for
- $\mathcal{C}_{eff}$ 3. Compute  $T_{out}$  for the given  $C_{eff}$  and  $T_{in}$
- 4. Compute  $\beta$
- 5. Compute  $\gamma$  from  $\alpha$  and  $\beta$
- 6. Find new  $C_{eff}$
- 7. Go to step 3 until  $C_{eff}$ converges













*R. Macys and S. McCormick, "A New Algorithm for Computing the "Effective Capacitance" in Deep* Sub-micron Circuits", Custom Integrated Circuits Conference 1998, pp. 313-316

## Summary

Delay model

- Elmore Delay model
- S2P model
  - Reduce the RC network to a 2-pole model
  - AWE is adopted for MOR
- Gate delay:
  - look-up table, k-factor approximation,
  - effective capacitance



## References

- R. Macys and S. McCormick, "A New Algorithm for Computing the "Effective Capacitance" in Deep Sub-micron Circuits", *Custom Integrated Circuits Conference* 1998, pp. 313-316
- J. Qian, S. Pullela, and L. T. Pileggi, "Modeling the "effective capacitance" for the RC interconnect of CMOS gates," IEEE Trans. on Computer-Aided Design of Integrated Circuits and Systems, vol. 13, pp. 1526-1535, Dec. 1994.
- Jason Cong , Lei He , Cheng-Kok Koh , Patrick H. Madden, Performance optimization of VLSI interconnect layout, Integration, the VLSI Journal, v.21 n.1-2, p.1-94, Nov. 1996 (Section 2.1-2.2)
- W. C. Elmore, "The Transient Response of Damped Linear Networks with Particular Regard to Wideband Amplifiers", Journal of Applied Physics, 1948.
- Jorge Rubinstein, and etc. "Signal Delay in RC Tree Networks", TCAD'83
- Emrah Acar, Altan Odabasioglu, Mustafa Celik, and Lawrence T. Pileggi. 1999. "S2P: A Stable 2-Pole RC Delay and Coupling Noise Metric". In Proceedings of the Ninth Great Lakes Symposium on VLSI(GLS '99).