

ASPDAC Tutorial: Power, Timing & Signal Integrity in SoC designs Section II

Eli Chiprout

Strategic CAD, Intel Labs


Chandler AZ

eli.chiprout@intel.com

Section II: Modeling, noise, timing

- The goals of this section is to:
 - Introduce scaling and the impact on models
 - Discuss the “interconnect problem”
 - Timing, noise, noise on timing
 - Give types of models used
 - Delay models
 - Moment models
 - PEEC models
 - Show inductance effects on-chip
 - Impact on modeling
 - Discuss model reduction


Design Paradigm Shift

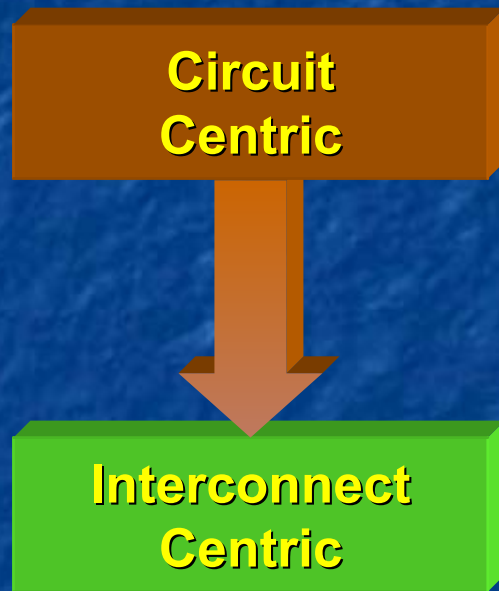


- **Circuit-centric**
 - Circuit poses major constraints
 - Slower convergence when interconnects weigh more
- **Interconnect-centric**
 - Interconnect dominated
 - Circuit built around interconnects



Interconnect scaling

 


Models also scale...

 

Trend of interconnect effects

Resistance

 

■ Resistance

- Very local
- Only varies at high F


Electric field



■ Capacitance:

- ◆ Electric field coupling
- ◆ Very small and well defined interaction zone

Magnetic field

 


■ Inductance:

- ◆ Magnetic field coupling
- ◆ global interaction zone

Opposed to digital design!


With more scaling?...

 

Line Inductance


Mutual Inductance

Timing Variation Due to Parasitics

 


- Interconnect parasitic variation impacts delay
- Easiest of the interconnect effects to solve and include
 - Delay formulas
 - Simplified model synthesis
 - Model reduction

Timing Variation Due to Coupling

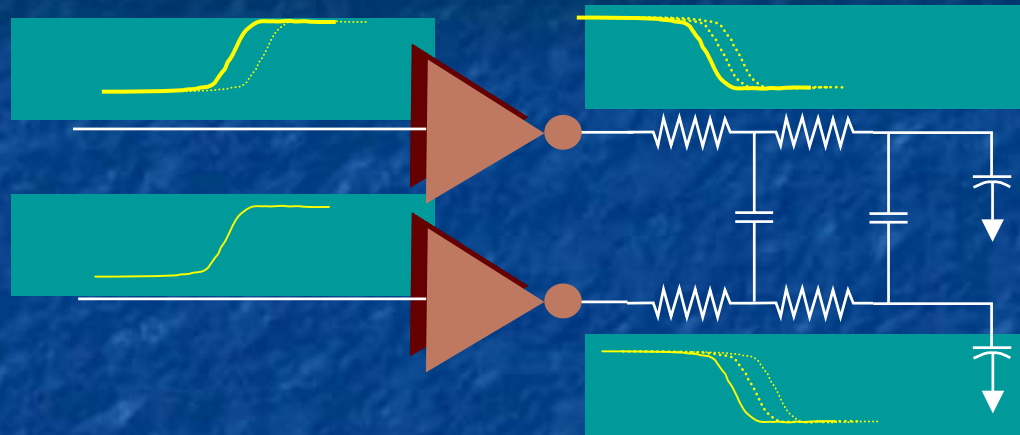

- Coupling variation increases delay variation (noise-on-timing)
 - Dynamic environmental variation
 - Interconnect coupling is spatially deterministic (fixed)
 - Patterns are temporally non-deterministic (usually)
 - Compare to process variation which is static (both spatially deterministic and non-deterministic)
- Analysis is more difficult because models extend the neighborhood of interaction (timing is path-based)

Noise Due to Coupling

 

- Coupling increases noise
 - Change signals away from being digital
 - Coupling can be capacitive (important and probable) or inductive (can be more important, less probable)
 - Somewhat simpler analysis than noise-on-timing
 - victims assumed to be static
 - noise can be approximately linearly additive


Chip-level design

- Increasing effects on delay, timing and noise-on-timing from electric fields
- Design has become increasingly interconnect-heavy
 - R(L)C Interconnects form the majority of models and flood our design databases with 1,000,000's of elements!


Overwhelming!

- Need to understand the modeling and when it is needed and when it is not

Lumped and Distributed RC Models

 

Lumped RC

 

Distributed RC

- Interconnect RC delay modeled by lumped RC model or distributed RC model
- Lumped: all C is combined into **one** capacitor and all R is combined into **one** resistor regardless of length of line or value of load
- Distributed: series of R and C lumped components – more elements, but more accurate
 - typically 3-5 can give a high degree of accuracy

Elmore Delay Modeling

- Elmore characterized interconnect lines as a lumped T section with resistor and capacitor elements.
- Elmore delay equation (for one line C and R):

$$T_d = \frac{1}{2} RCl^2 + RC_L l + R_D Cl + R_D C_L$$

- R is the resistance per unit length
- C is the capacitance per unit length
- l is the interconnect length
- R_D is the driver resistance
- C_L is the load capacitance

Sakurai Delay Modeling

- Sakurai studied distributed RC lines and modified Elmore delay equation for accuracy
- Sakurai delay equation:

$$T_d = 0.377RCl^2 + 0.693(RC_Ll + R_DCl + R_D C_L) *$$

- Low 100's MHz: these models predict circuit behavior
- In gigahertz regime: these models may be inadequate

*error in the handout – see T. Sakurai, et al., "Approximation of wiring delay in MOSFET LSI", IEEE Journal of Solid-state circuits, Vol. SC-18, No. 4, Aug. 1983.

RC Parasitics at Medium Frequencies

- Low frequencies, skin effect on resistance negligible - R considered frequency independent.
- If $R \gg \omega L$, L neglected and RC model adequate
 - R is interconnect resistance
 - L is interconnect inductance
 - ω is operating frequency
- Smaller features and higher frequencies - R and C affected by technology scaling in relation to line width.

Skin-effect & Skin depth


- Skin-effect increases R and reduces L

$$\delta = \frac{1}{\sqrt{\pi \cdot f \cdot \mu \cdot \sigma}}$$

- σ is conductivity
- μ is permeability
- f is sig. frequency

Very little current

Most of the currents

 

- Skin-depth is the point at which current density inside a conductor decays to 1/e the surface value
- Skin effect typically occurs when the skin-depth approaches 1/2 the width or thickness of the conductor
- Not much skin effect on-chip unless thickness is large, modeling usually not done

When to Use RLC Modeling

- Check 1: Line cap-dominated $C_L < \frac{1}{8} Cl$
 - Cl = load capacitance, C = per-unit-length coupling capacitance, l = length of the line
- Check 2: Line under-damped $\frac{Rl}{2} \leq \sqrt{\frac{L}{C}}$
 - l is length of interconnect
 - R is per-unit-length-resistance
 - L is per-unit-length self-inductance
 - C is per-unit-length coupling capacitance
- Check 3: Z magnitude $2\pi f_s Ll > \frac{Rl + Z_{DRV}}{2}$
 - Z_{DRV} is driver impedance
 - f_s is **significant** signal frequency based upon rise time
 - Is inductive impedance comparable to line resistance and driver impedance?

Multi-conductor RLC Modeling

- In general interconnects & power delivery systems with N number of conductors can be modeled using a system of NxN RLC matrices
- For each interconnect line, a corresponding row and column exists in the [R] matrix, [L] matrix, and [C] matrix.
 - G matrix is generally neglected in $Z=(R+sL)/(G+sC)$
- The off-diagonal terms represent the interaction or coupling between two interconnects
- A complete set of matrices (RLC) can be extracted for any given frequency by 2D EM modeling

Why Multi-conductor RLC Modeling?

- Multi-conductor modeling is expensive to use but always accurate
- For some n wire structures, the return path assumption can be applied to reduce to $n-1$
- Typically used for board level but also for detailed understanding (not full-chip flows)
- Common applications:
 - To analyze detailed noise coupling between groups of signals that switch simultaneously (i.e., a bus)
 - To analyze V_{CC} & V_{SS} return effects

Why think about inductance?


- **NEW TECHNOLOGY**
 - Fast switching times
 - Every pico-second is important in fast designs pushing limits
- **SILICON** observations
 - Divergence between silicon measurements and RC models
 - HP documented uP silicon failure due to inductance
- **SIMULATION** observations
 - Noise difference between RC and RLC models
 - Timing difference between RC and RCL models
 - Skew difference between RC and RLC models
- **SPEED OF LIGHT** limitations
 - We are approaching these regimes on chip so inductive effects must appear

Primary effects of on-die inductance


- **Power grid noise (up to resonance):**
 - **di/dt rapidly grows per new technology**
- **Clock skew**
 - **inductance especially important due to wide wires and fast edges**
- **Delay (slope at receiver end):**
 - **under- or overestimated if inductive coupling is ignored**
 - **underestimated if return path resistance is neglected**
 - **impacts repeaters insertion methodology**
- **Propagation delay (flight time):**
 - **ignored (estimated as 0) if interconnect inductance is ignored;**
 - **(LC) per unit length $\geq \mu\epsilon = 1/v^2$, v = speed of light in matter**
 - **SiO₂: $\epsilon/\epsilon_0 = 3.5$, $v = 160 \mu\text{m/psec}$, $\sim 10,000 \mu\text{m} / 60 \text{psec}$**
- **Overshoot-ringing:**
 - **severe reliability hazard**
- **Mutual noise:**
 - **mutual inductance can, on low probability, be higher than cross-cap noise**

Inductive Effects

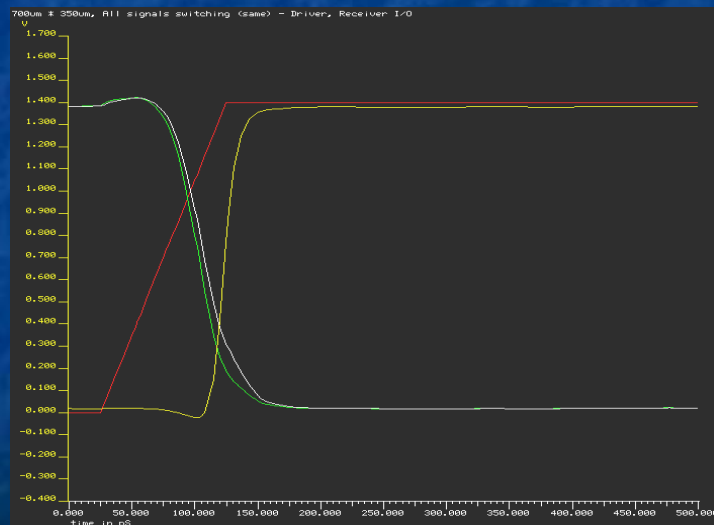- Impact on signal nets
 - Oscillations, under/over shoot
 - inductive cross-talk
 - Increase in signal delay
 - reduction in transition time




RC - MODEL

 


RLC -
MODEL

Noise input to the receivers for WC

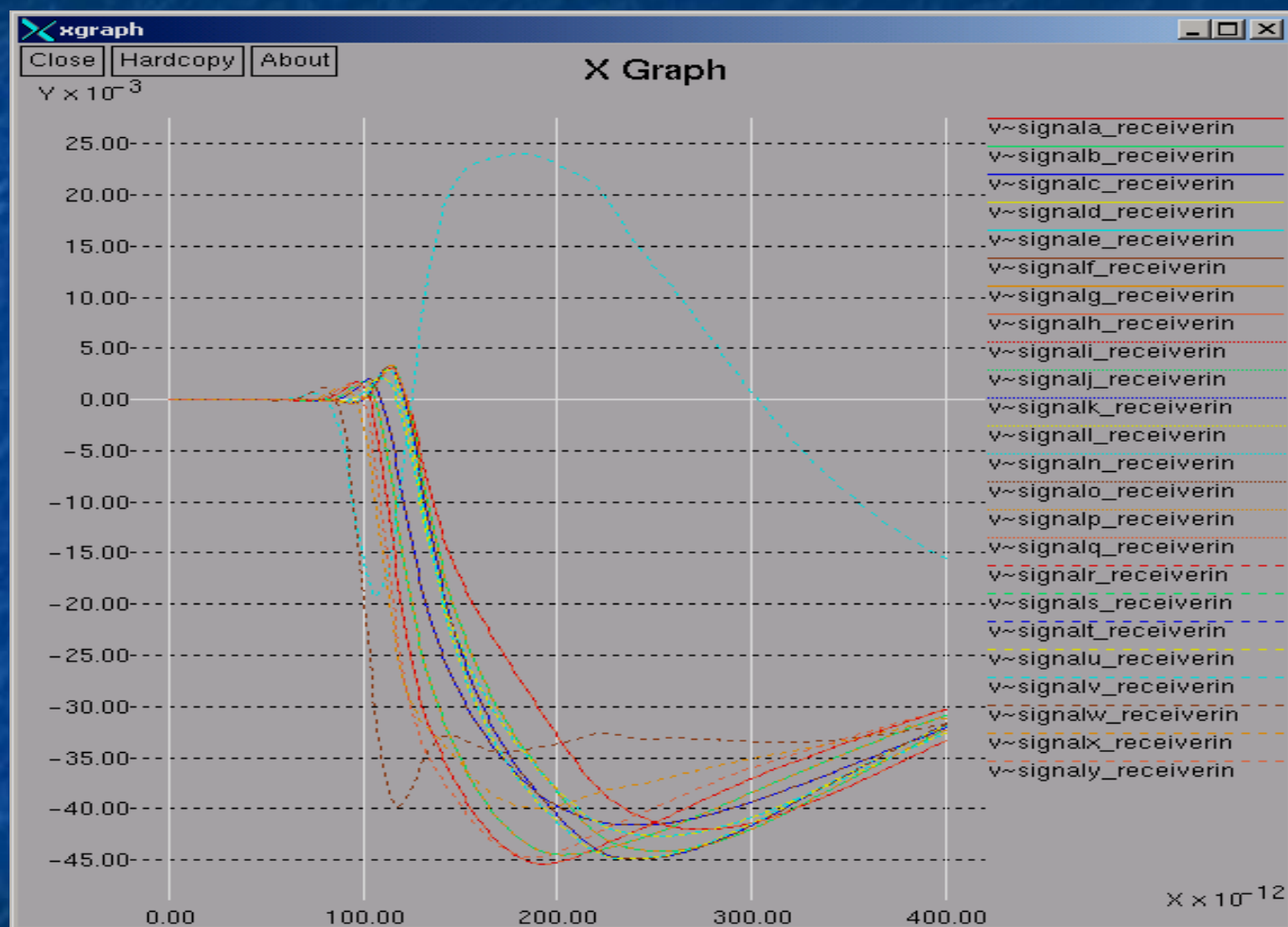


RC/RLC noise difference

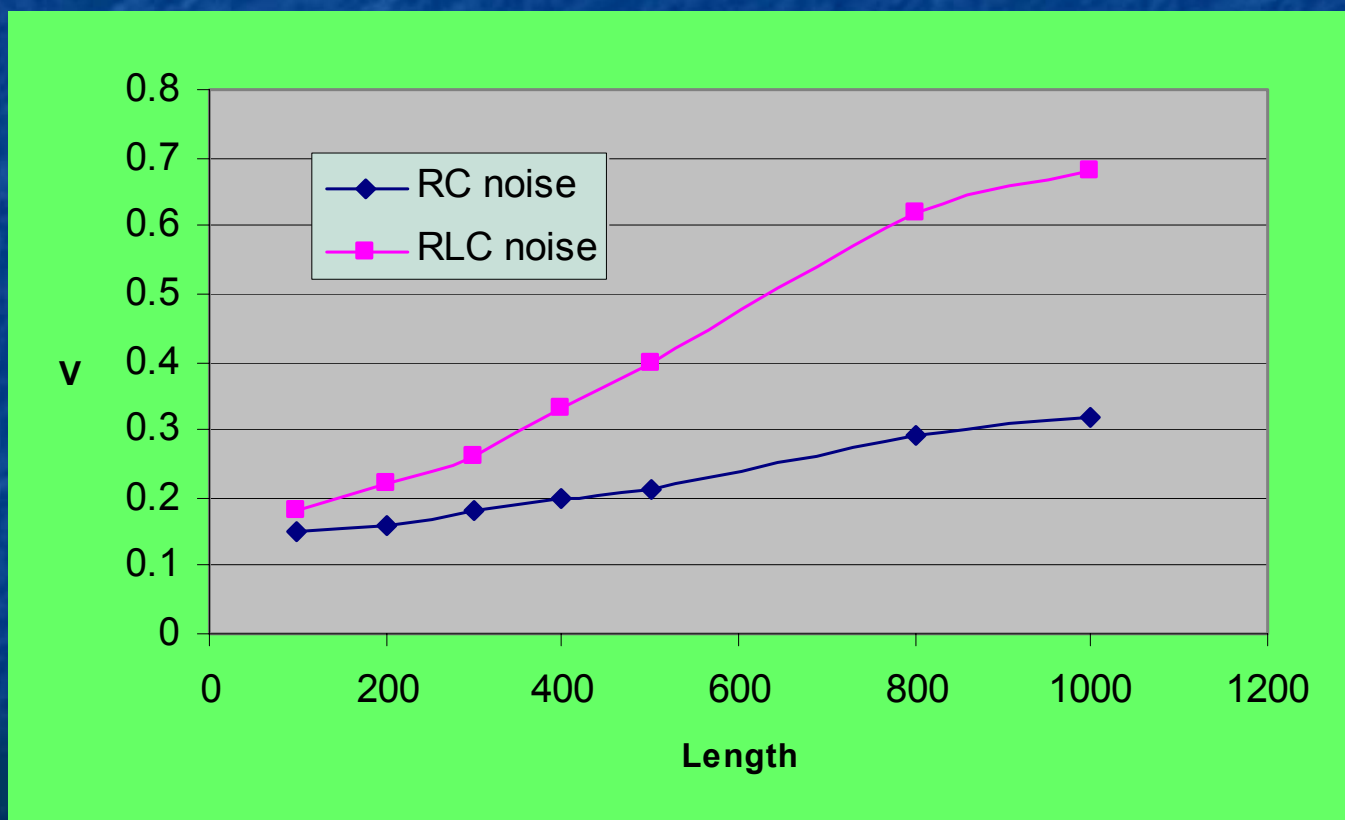Rise time of the order of 30ps yielding noise



Noise

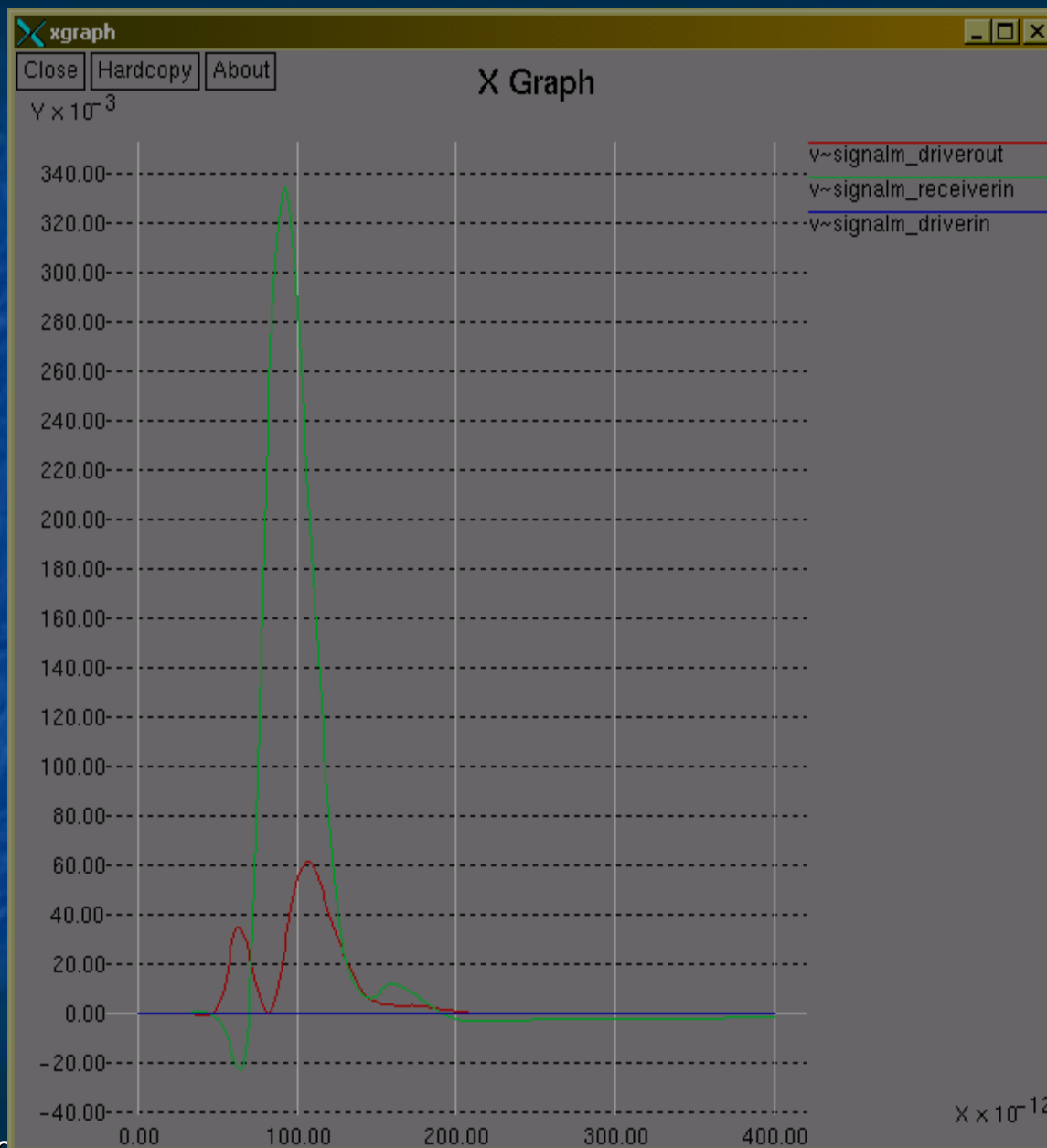


1000u line

25 signals

Victim at 0V

WC RLC noise (+)

Timing

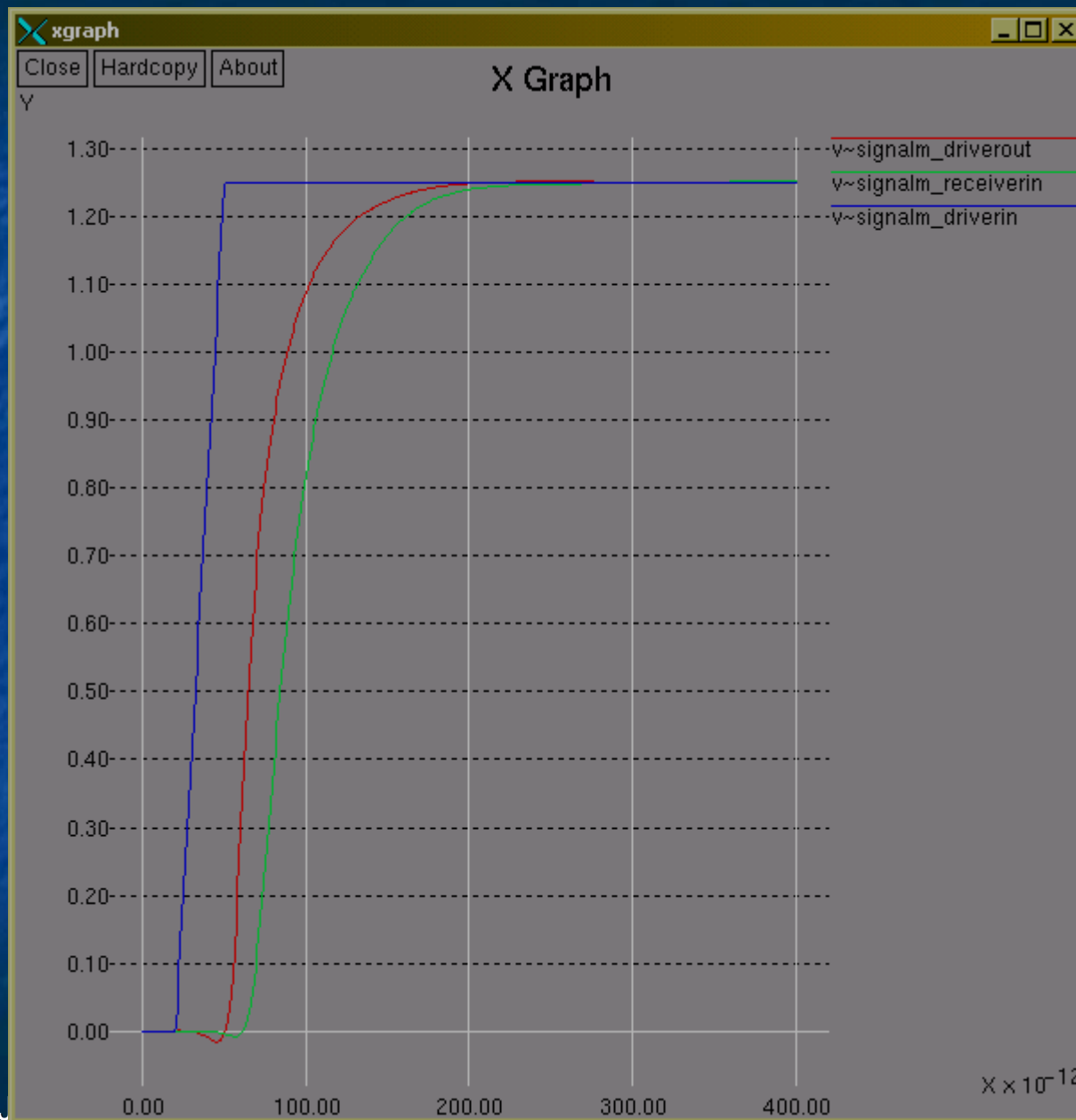


1000u line

25 signals

Victim up

NO RLC noise

Timing

 


1000u line

25 signals

Victim up

WC RLC noise (+)

Timing

 


1000u line

25 signals


Victim up

WC RLC noise (-)

Window of influence

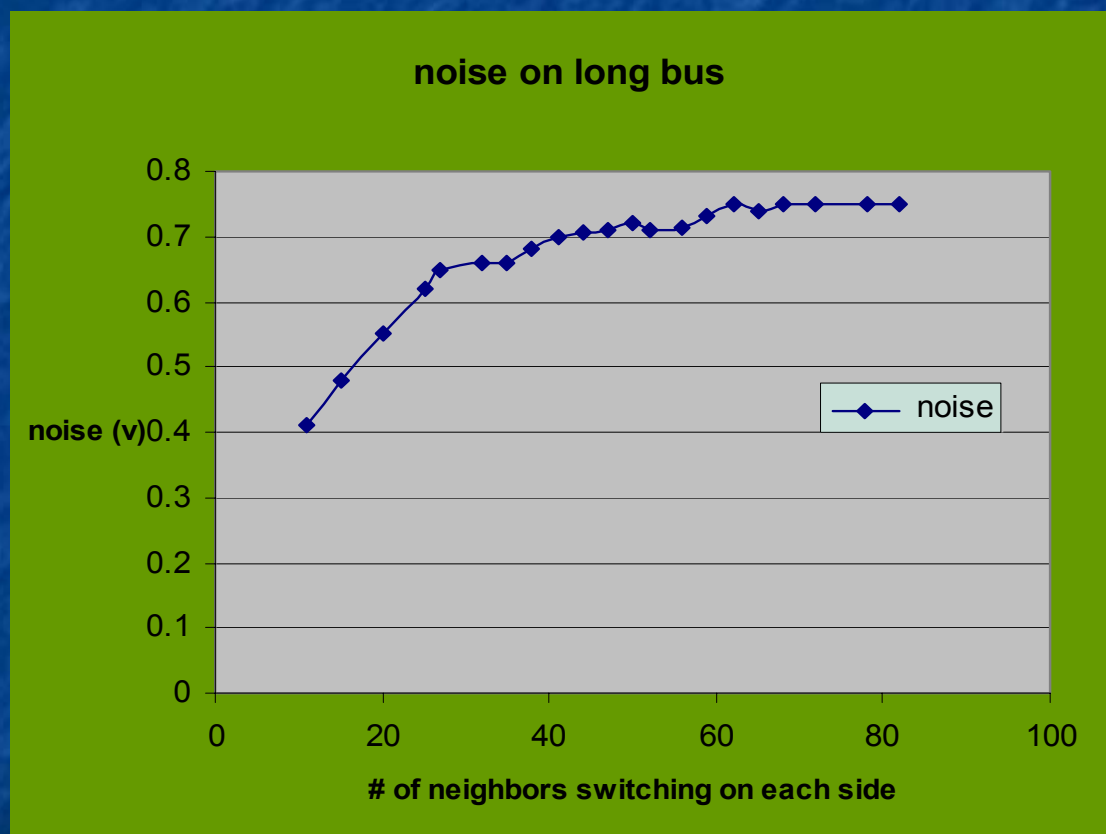

On-chip interaction: complex attack

 

Inductive neighborhood summary


- Inductive attackers in a large neighborhood
 - On same layer
 - On other layers
 - If wrong way wires, not only on parallel wires
- Returns influence in a large neighborhood
 - Width and location of returns important

This gives rise to complexity – much more than capacitive extraction!


Multiple attackers

- Worst case scenario is terrible!
- If we used this, design could not be done
- Probability of worst case is almost zero
- However, a reasonable probability window must be chosen by designers
- **This choice of probability window can be the source of inaccuracy greater than inductive modeling!**
- Complexity – not accuracy.

Top metal delay: driver output

 


Top metal slew: receiver input

 

Overview of PEEC


- “Equivalent circuit models for three dimensional multiconductor systems”, IEEE Trans. MTT, A. E. Ruehli, 1974.
- The PEEC approximation is based upon the proper electromagnetic interpretation of the various terms in the electric field integral equation (EFIE)
- Elements in the resulting matrix solution are related to equivalent circuit elements which can be incorporated into a non-linear circuit simulator.
- The main advantages of this approach are
 - output is a SPICE netlist
 - Ability to model any electromagnetic interaction
 - Excellent for understanding of basic signal, power grid, clock effects
- The main disadvantages are
 - Too detailed for most on-chip applications

Discretization for PEEC

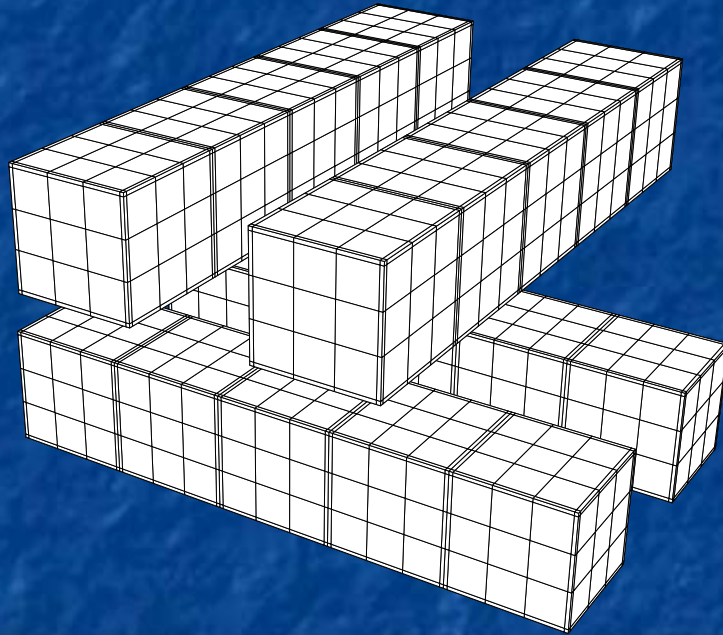

3D PEEC Model

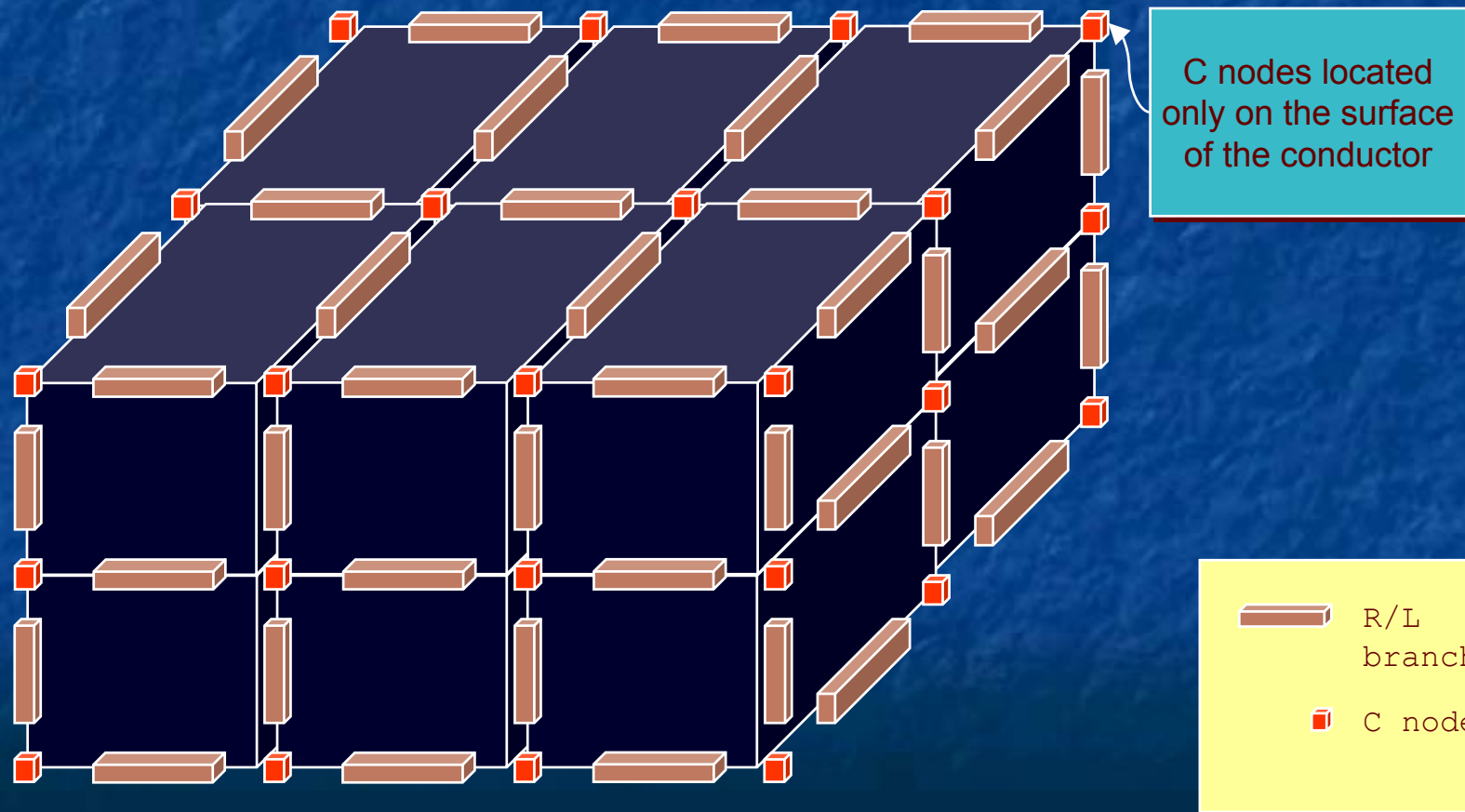- In general, conductors are modeled using a 3D PEEC model where current flows in x-, y-, and z-directions



Overview of the PEEC Concept

- The vector and scalar potential functions


$$\bar{A}(\bar{r}, t) = \frac{\mu}{4\pi} \sum_{k=1}^K \int_{v_k} \frac{\bar{J}(\bar{r}', t - |\bar{r} - \bar{r}'|/c)}{|\bar{r} - \bar{r}'|} dv'$$

$$\Phi(\bar{r}, t) = \frac{1}{4\pi\epsilon} \sum_{k=1}^K \int_{v_k} \frac{q(\bar{r}', t - |\bar{r} - \bar{r}'|/c)}{|\bar{r} - \bar{r}'|} dv'$$

$$\frac{\bar{J}(\bar{r}, t)}{\sigma} + \frac{\mu}{4\pi} \frac{\partial}{\partial t} \sum_{k=1}^K \int_{v_k} \frac{\bar{J}(\bar{r}', t')}{|\bar{r} - \bar{r}'|} dv' + \frac{1}{4\pi\epsilon} \sum_{k=1}^K \nabla \left[\int_{v_k} \frac{q(\bar{r}', t')}{|\bar{r} - \bar{r}'|} dv' \right] = 0$$


along with $J = \sigma E$ are substituted into the EFIE, resulting in

Basic PEEEC cell

 

- The charge density, q , and current density, J , are discretized into **capacitive** and **inductive/resistive** cells, respectively

PEEC: basic circuit

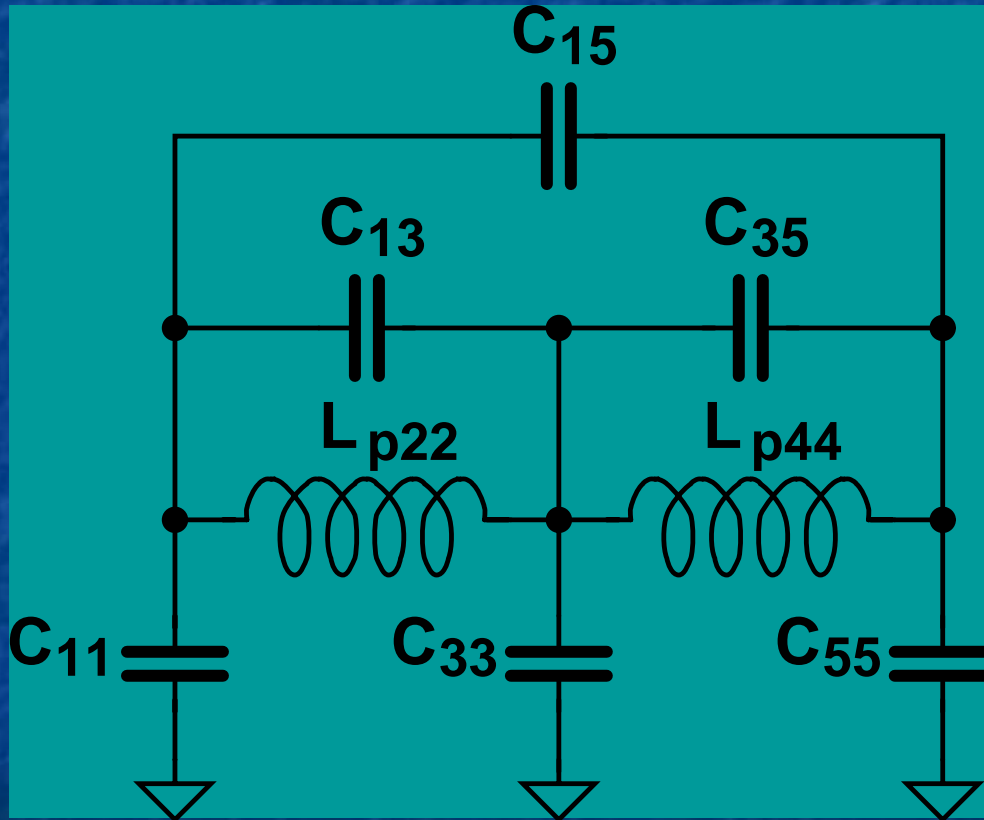

The MR problem

- Circuit simulators (e.g. Spice) simulate nonlinear networks well but at high cost
- Extraction, packaging and interconnect modelling generate large linear (RLC) networks (especially in high speed GHz logic, clock and packaging design)
- Nonlinear simulators too slow to simulate large linear networks



MR Requirements

- Reduce large linear networks for standalone time/frequency domain simulation
- Reduce and macromodel large linear networks for nonlinear simulation
- reduction with error control, and simulation transparently to the user
- Applicable to on-chip logic interconnect, clock, power and gnd nets, packaging pin and interconnect models
- tricky mathematical techniques necessary to accomplish this for all frequency ranges

MR: AWE approach

$$I(s) = H(s)V(s)$$

$$I(s) = (H_0 + H_1s + H_2s^2 + \dots)V(s)$$

$$I(s) = \left(\frac{a_0 + a_1s + a_2s^2 + \dots + a_{q-1}s^{q-1}}{b_0 + b_1s + b_2s^2 + \dots + b_qs^q} \right) V(s)$$

$$I(s) = \left(\sum_{i=1}^q \frac{k_i}{s - p_i} \right) V(s)$$

$$i(t) = \left(\sum_{i=1}^q k_i e^{p_i t} \right) * v(t)$$

Problems with AWE

- Moments generated loose accuracy
- The number of poles is limited (may be ok for RC)
- Order of approximation is not chosen automatically (no idea about the error)
- Macromodelling not in block form in existing codes
- Krylov subspace provides greater range of accuracy for same initial cost as in AWE (DC decomposition)
- Block algorithm make MIMO possible
- Automatic error control for order of approximation based on residual

Krylov based iteration

$$\begin{aligned} E\dot{x} &= Ax + Bu \\ y &= C^T x + Du \end{aligned}$$



$$\begin{aligned} \hat{E}\hat{x} &= \hat{A}\hat{x} + \hat{B}u \\ \hat{y} &= \hat{C}^T \hat{x} + \hat{D}u \end{aligned}$$

$$\text{span}\left\{(A - \sigma E)^{-1} B, (A - \sigma E)^{-1} E (A - \sigma E)^{-1} B, ((A - \sigma E)^{-1} E)^2 (A - \sigma E)^{-1} B, \dots\right\}$$

$$\Rightarrow V_j$$

- V is an orthogonal subspace

$$V_j^T (A - \sigma E)^{-1} E \hat{x} = V_j^T (A - \sigma E)^{-1} A V_j \hat{x} + V_j^T (A - \sigma E)^{-1} B u$$

$$\hat{y} = C^T V_j \hat{x} + D u$$

Residual based stopping criterion

$$X(s) = (sE - A)^{-1} B$$

Actual frequency response

$$\hat{X}(s) = V_j (s\hat{E} - \hat{A})^{-1} \hat{B}$$

Approximate response

$$error = C^T (X(s) - \hat{X}(s))$$

Actual error (expensive!)

$$\hat{R}(s) = (sE - A)\hat{X}(s) - B$$


Residual error (cheap!)

$$= (sE - A)V_j (s\hat{E} - \hat{A})^{-1} \hat{B} - B$$

- residual error has a frequency indep component which gets calculated only once for a given model order and freq dependent component which is inexpensive to calculate for entire freq range
- residual weighted to get low freq and DC accuracy

Passivity

- Are stable systems a closed set? NO!

 

References and further study

- M. Celik, L. Pileggi, et al., "**IC Interconnect Analysis**", Kluwer academic, 2002
- ""Inductance 101: analysis and design issues", K. Gala, D. Blaauw, J. Wang, V. Zolotov and M. Zhao, DAC, June 2001
- M. W. Beattie and L.T. Pileggi, "Inductance 101: Modeling and extraction", DAC, June 2001
- A. E. Ruehli, "Inductance calculation in a complex integrated circuit environment", IBM Journal of Research and Development, pages 470-481, Sept. 1972.
- J. Rubinstein, P. Penfield and M.A. Horowitz, ``Signal Delay in **RC** Tree Networks," IEEE Trans. Computer-Aided Design, vol. CAD-2, No. 3, pp. 202-210, July 1983.
- C. J. Alpert, A. Devgan, and C. V. Kashyap, "RC delay metric for performance optimization", IEEE Trans. on CAD, 20(5):571-582, May 2001
- W. C. Elmore, "the transient response of damped linear network with particular regard to wideband amplifiers." J. Applied Physics, p. 55-63, 1948.
- A. Devgan, "Efficient coupled noise estimation for on-chip interconnects", ICCAD 1997, p. 147-151.